



Specialists in electronic kits, components and products.

## KD6100: KIT - LOGIC PROBE DY10/17

DIYODE Magazine Oct 2017 (p58 to p67).

Rev 1

Batch No:

### PLEASE READ BEFORE COMMENCING CONSTRUCTION

The guarantee on this kit is limited to the replacement of faulty parts only, as we cannot guarantee the labour content you provide. Our Service Department does not do general service on simple kits and it is recommended that if a kit builder does not have enough knowledge to diagnose faults, that the project should not be started unless assistance can be obtained. Unfortunately, one small faulty solder joint or wiring mistake can take many hours to locate and at normal service rates the service charge could well be more than the total cost of the kit.

If you believe that you may have difficulty in building this kit (which is simply a complete set of separate parts made up to a list provided by the major electronics magazines) and you cannot get assistance from a friend, we suggest you return the kit to us IN ITS ORIGINAL CONDITION for a refund under our satisfaction guarantee.

Unfortunately, kits cannot be replaced under our satisfaction guarantee once construction has been commenced.

#### CONTACTS:

For queries with regards to the design aspects of this project please contact the Project Designer. It is recommended to check the designers/publishers website for further updates since this document was issued. DIYODE Magazine, PO Box 546, Gosford NSW 2250 Australia.  
Tel: +61 (2) 4326 0160, web: [www.diyodemag.com](http://www.diyodemag.com), email: [help@diyodemag.com](mailto:help@diyodemag.com)

For quality issues please contact the Production Manager at Jaycar Electronics and provide the following information:

- Product Number
- Batch No
- Details of Quality Issue

#### Notes and Errata (at time of print):

Jaycar Electronics:

- uses netlists to confirm that the PCB artwork matches the schematic(s) and parts list(s) published. Observed variations are verified and incorporated into the kit but may not be published by DIYODE Magazine.
- upgrades the original PCB design to use component footprints, possible component shape, value and lead configuration alternatives and aligned polarized components where possible. You may wish to bend component leads and use component pads further apart.
- has updated the project article with relevant notes and errata. It will therefore differ from the original article published in the magazine.
- recommends to check the designers/publishers website for further notes and errata since this document was issued, before starting construction.

## KD6100: KIT - LOGIC PROBE DY10/17

Rev 1

#### Possible Substitutions

Original Part	Original Part Desc	Subst Part	Subst. Part Desc.
N/A			

#### PARTS LIST

Please note that catalogue numbers refer to suitable products from the Jaycar product range. Quantities listed refer to the actual number of items required. When purchasing items separately, take pack quantities into account.

<sup>1</sup> See section about Substitution <sup>2</sup> See section about Notes & Errata <sup>3</sup> Processed Panel not part of Case listed  
Catalogue numbers starting with "E" or listed as "Special Order" (incl. processed panels) are Kit specific and may not be readily available.

For queries with regards to the design aspects of this project please contact the Project Designer at: DIYODE Magazine, PO Box 546, Gosford NSW 2250 Australia.

Tel: +61 (2) 4326 0160, web: [www.diyodemag.com](http://www.diyodemag.com), email: [help@diyodemag.com](mailto:help@diyodemag.com)

For additional code, or to discuss this project, visit: <https://diyode.io/004tdqg>

#### RESISTOR(S)

Cat.#	Qty*	Description	Component Ident And/Or Location
RR0536	2	RES 0.5W MTL 33R 1%	Orange Orange Black Gold Brown
RR0560	1	RES 0.5W MTL 330R 1%	Orange Orange Black Black Brown
RR0572	2	RES 0.5W MTL 1K0 1%	Brown Black Black Brown Brown
RR0588	1	RES 0.5W MTL 4K7 1%	Yellow Purple Black Brown Brown
RR0594	3	RES 0.5W MTL 8K2 1%	Grey Red Black Brown Brown
RR0602	1	RES 0.5W MTL 18K 1%	Brown Grey Black Red Brown
RR0616	1	RES 0.5W MTL 68K 1%	Blue Grey Black Red Brown
RR0620	5	RES 0.5W MTL 100K 1%	Brown Black Black Orange Brown
RR0628	1	RES 0.5W MTL 220K 1%	Red Red Black Orange Brown
RR0644	4	RES 0.5W MTL 1M0 1%	Brown Black Black Yellow Brown
RR0660	1	RES 0.5W MTL 10M 1%	Brown Black Black Green Brown
RR1654	1	RES 0.25W CARB 1M8 5%	Brown Grey Green Gold

#### CAPACITOR(S)

Cat.#	Qty*	Description	Component Ident And/Or Location
RE6032	1	CAP ELECT RB 1U 63V 105C P=2MM 5X11MM	1uF / 63V
RM7010	1	CAP MKT 1N 100V P=5MM 7.5X2.5X6.5MM	1.0n / 1n0 / 102

#### SEMICONDUCTOR(S)

Cat.#	Qty*	Description	Component Ident And/Or Location
PI6501	1	SKT IC TIN/G 14PIN/300MIL	
ZD0100	1	LED 3MM DIF RED 40MCD	
ZD0119	1	LED 3MM DIF ORG 40MCD	
ZD0120	1	LED 3MM DIF GRN 40MCD	
ZL3339	1	IC LM339N/LM2901N QUAD COMPARATOR DIP14	LM339N/LM2901N
ZR1004	1	DIODE 1N4004 400V 1A DO41	1N4004
ZR1100	2	DIODE 1N914/1N4148/BAW76 DO35	1N914/1N4148/BAW76
ZT2152	1	TRAN BC547 NPN 50V 100MA TO92	BC547
ZT2164	1	TRAN BC557 PNP 50V 100MA TO92	BC557

#### HARDWARE / WIRE(S) / MISCELLANEOUS

Cat.#	Qty*	Description	Component Ident And/Or Location
Spec Order	1	PAPERCLIP 33MM	cut & use as probe tip
EN3082	1	SOLDER 60/40 1MM 50CM	
HM3040	1	HOOK EZ 55MM RED	
HM3041	1	HOOK EZ 55MM BLK	
SS0823	1	SWITCH SLIDE SMIN PCB DPDT	

#### HARDWARE / WIRE(S) / MISCELLANEOUS (LOOSE)

Cat.#	Qty*	Description	Component Ident And/Or Location
EC8411	1	PCB (KD6100) PTH SM NTN 89X27MM	double sided, soldermask, overlay
WB1702	25cm	CABLE SPKR FIG8 GRY&BLK L/D	

# Design And Make: The Ubiquitous Logic Probe

**This is the first of our discrete projects! A logic probe is a powerful tool for any maker to have, since it simplifies debugging and testing. - by Bob Harper**

Why do we use logic? Because all modern computers use logic. To not use logic would be illogical!

Logic sometimes fails, however, when the analog levels that control the inputs to gates, or the loading on the outputs, cause a misunderstanding. Logic works when the signal levels comply with logical requirements, (i.e., standards).

## TESTING LOGIC AT THE HOBBY LEVEL

Many years ago I learned logic as a means to control stage lighting for rock bands. I knew electronics, but had never even heard of TTL or any of the digital logic technologies, except for switches and relays as I was, at that time, an apprentice electrician.

Later on I used logic ICs, 74xx devices in my first computer that consisted of seven ICs. It didn't take much more circuitry before I needed something better to test these circuits. Eventually I saw some articles about logic probes and built one, using just four transistors and a few resistors. Recently I was asked if I could make a logic probe and that is where this story began.



## MAKER LOGIC

Robotics, 3D printers, CNC mills, routers, and so on are all applications of the inputs and outputs of computers, being used to drive mechanical and opto-electric devices. The logic analyser is a terrific instrument, but overkill; and usually over-priced for hobbyists. Multimeters often have a logic function, but they can be slow, insensitive, and inaccurate. They can also be inconvenient; for example when you're trying to hold a probe on a tiny pin, and you need to avoid touching the many other tiny pins that sit around it, when looking back and forth at the meter.

### HOW IS A LOGIC PROBE BETTER THAN A MULTIMETER?

The logic probe has two or three coloured LED indicators near the probe tip, so the user can see the result without looking away. It also clearly shows three conditions using two of those LEDs. Also, multimeters read logic "0" or logic "1", but not all meters can handle levels in between. Therefore, they may make mistakes in interpreting an open circuit or dead gate.

### WHAT DOES A GOOD LOGIC PROBE NEED TO DO?

As we mentioned, typically logic probes read logic "0" and logic "1". This may sound simple, but it's not necessarily the case.

Firstly, it will help to know what type of system it will be used on. On some logic systems, the probe would read up to 48V for a logic "1" on relay logic, and perhaps +/-12V on other systems. Many systems have existed, most are now gone, relay, DTL, ECL and so on.

So let us begin by defining our logic probe as intended for TTL. You might say 0 volts for logic "0", which although commonly agreed with, is not completely correct. In fact, most systems never actually reach exactly 0V. The truth is, TTL accepts from 0V to 0.8V as meaning a logic "0", and CMOS accepts 0V to 1.5V as logic "0", at least on a system with 5V rail voltage (and up to 4V on a system with 15V rail voltage). Then, we realise that the Arduino, along with many other computer systems, use either 5V or 3.3V rail voltage as a modern option. Thankfully, a 3.3V system still uses TTL levels for logic "0" (i.e., 0.8V).

The output voltages are another issue. TTL, either 5V or 3.3V systems, expect the output voltage to be from 0V to 0.5V, while the CMOS system expects the output voltage to be less than 0.05V – the main reason for lower power requirement of CMOS.


Logic "1" levels for TTL inputs (both 5V and 3.3V systems) need to be greater than 2V; but for CMOS, on a 5V supply, the inputs need to be above 3.5V to be a valid "1".

So a professional probe requires a different design for each system, or a switch to select the system in use. For hobbyists, unless chasing a glitch at the very edge of a system, or attempting maximum "fan-out" (loading), where noise can cause false logic, a hobbyist can suffice with 0V to 0.8V as acceptable logic "0", and above 2V as logic "1". In fact, a technician would probably pull out an expensive CRO or logic analyser by then anyway.
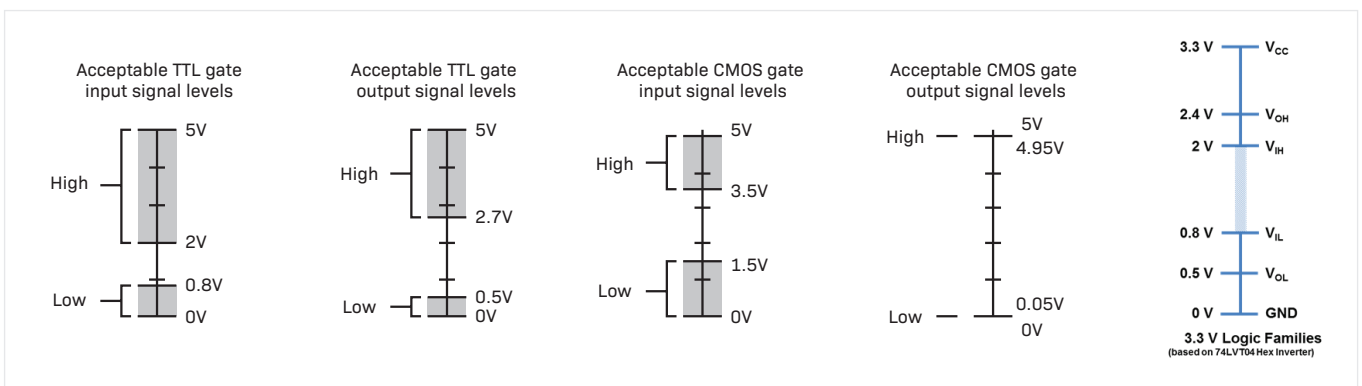
## LOGIC SHIFTS

In a system where the logic is 'state determined' and the outputs don't change unless an input is changed, logic "0" and logic "1" are quite sufficient. On low speed systems, a flickering pair of red and green LEDs might be enough to say the clock is ticking, but even experienced technicians have difficulty on faster systems. The main issue is knowing whether the system is clocking, or held in a high impedance state or centre voltage (i.e., between a logic "0" and a logic "1"). To identify this, a logic probe can have a 'pulse' LED, usually orange, that may simply light when oscillating, or flash at a fixed frequency when a pulsed signal or clock is running. Some probes have a function to 'catch' a transition, meaning that the orange LED turns on and latches on until reset.

If the probe tip changes logic, or even if the logic momentarily changes then returns to the initial state, whether correctly following the logic, or due to a glitch, the latch will pick it up. This is useful for catching sporadic and unintentional pulses that may trigger logic circuits intermittently, and especially if the circuit is triggered unexpectedly and unpredictably. >>



## » OUR LOGIC PROBE DESIGN

While we would be proud to say we designed a new type of logic probe, it would be very likely that somebody else had already published or uploaded something very close to this design, even if we have done all the hard work ourselves. Anyway, the first step most engineers would take is to research what has already been done. This circuit uses the best method we know of, using a simple IC, and for very little cost.


### WHAT DO I WANT?

Honestly? I want something easy to make, which will last forever and cost me nothing! Or as close to that as possible! With this in mind, I researched many existing designs, some as early as 1975, to try to compare approaches.

Hobbyists could easily get away with two LEDs and two resistors, and that approach is good when you need something cheap and/or fast! So long as you realise that you will be getting very basic results, and will be loading the circuit so much you might actually cause logic faults in the process.

So, as in all test instruments, we want the probe to take as little from the circuit as practically possible, and try to be sure that the voltages are within the limits shown in Figure 1 – at least for TTL and perhaps 3.3V TTL.

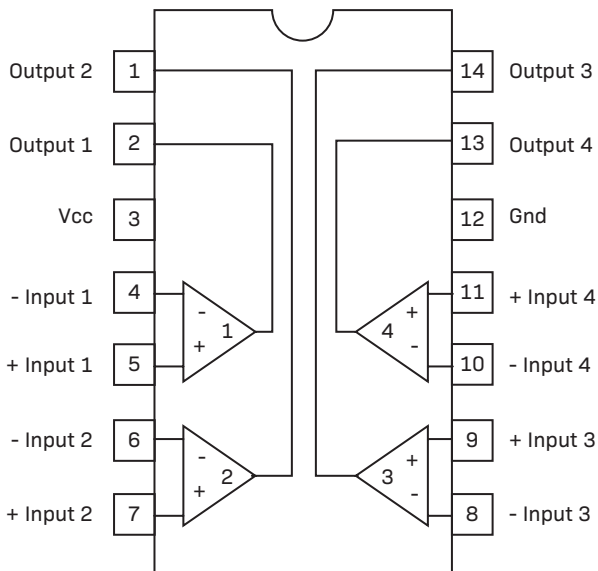Another factor can be the speed of operation, but hobbyists are usually happy with basic technology, so although high speed quad comparators were researched, we settled for an old friend that is easy to find, cheap, and has good manners: the LM339, which is also used in many of the designs already available on the internet and elsewhere.



## WHAT IS A COMPARATOR?

A comparator is a type of op-amp that compares the voltage on the two input pins, and decides which voltage is the highest. Then the output is changed to reflect that decision. Op-amps can do this, but are designed as analog devices on both input and output. Comparators are required to switch the output.

Comparators have a “-” input, and a “+” input, but either input can have a voltage anywhere between the supply voltages applied to them. The “+” and “-” do not refer to the voltage, but the effect the inputs have on the output.

DEVICE INPUTS	OP-AMP OUTPUT	OC COMPARATOR OUTPUT
+ input < - input	-ve value	Transistor Off
+ input = - input	Analogue	Switching
+ input > - input	+ve value	Transistor On


If the “+” is more positive than the “-”, the output turns on, but if the “-” is more positive than the “+” the output turns off.

Note that the output itself is a transistor with an open collector (OC), unlike most op-amps. OC simply means there is an NPN transistor with the collector connected to that output pin, and the emitter connected to ground via the power supply pins. Therefore, the output does not go high or low, simply on or off. You will need to connect the load between the OC output pin and a positive supply, which can be a separate supply to the IC supply itself.
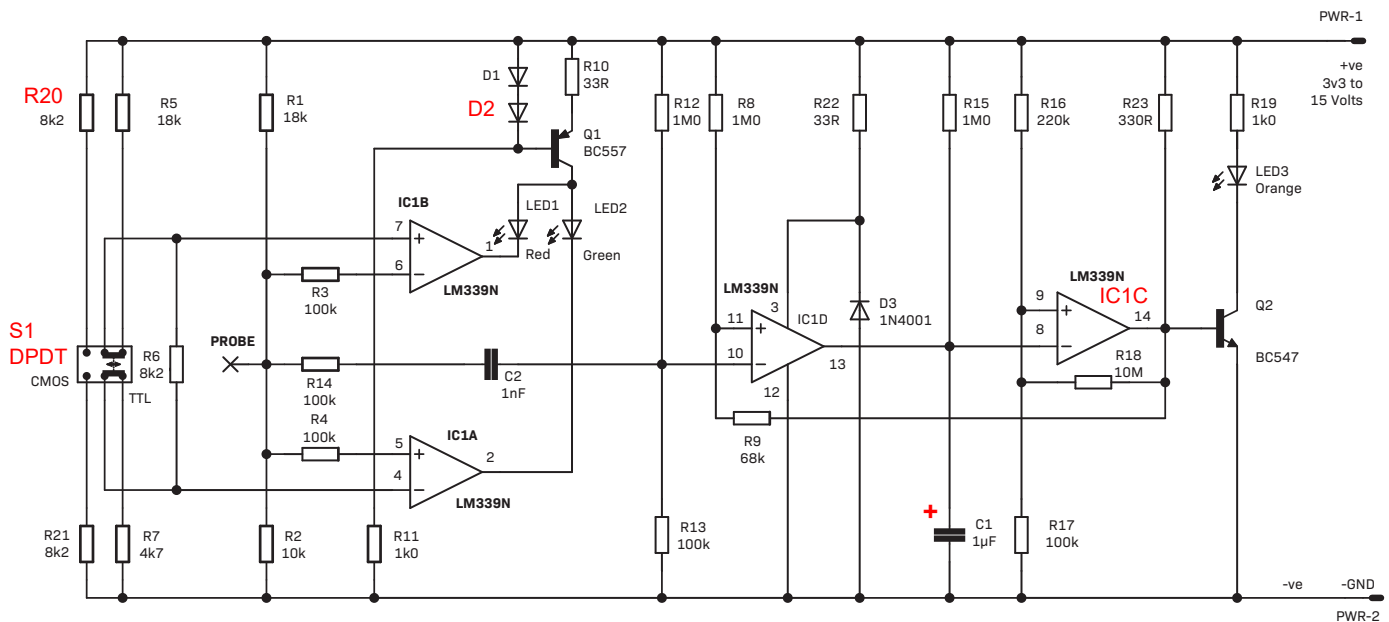
## LM339 QUAD COMPARATOR

The LM339 has four comparators (hence “quad”) in one 14-pin device; a DIP (dual inline package) device – a through-hole device – is my preference, but SMD and other versions are also available. The inputs do not require much current to detect the logic, typically 25nA (yes, that’s “nano amps”), and the whole device takes 0.8mA total power, regardless of supply voltage, which can be from 2V to 32V. (Note: that does not include the output loads as they are supplied by a separate power source external to the IC power pins.) Therefore, the LM339 will work on 3.3V and 5V TTL systems, as well as CMOS and some others, (with adjustments to some resistor circuit values if you are keen). The output is compatible with TTL, MOS and CMOS, and the current draw per output is rated at 20mA, which is sufficient for directly driving 3mm LED indicators.

Switching speed is the least impressive of the specifications, but only if you can see and think at almost 2MHz. In fact, the design doesn’t require that kind of speed even if the micro runs at 20MHz. The signals on the computer I/O lines will not normally be changing that fast, and pulses can still be detected. I do recommend that



The circuit of the Logic Probe and it's LM339 Quad Comparator core.

when you use any device, you download the datasheet/s and some application notes off the internet, and read them. It is a good way to determine what it all means, and at minimum the datasheets will tell you what pins to use.

## THE CIRCUIT

Take a look at Figure 2. Note what the pins are and try to remember them. Particularly note that pin 3 is the positive or VCC connection, 5V in most cases, and pin 12 is ground.

Each comparator has two inputs (+ and -) and one output. Note the polarity of the inputs on either side of the IC. Comparator 1 has its inputs on pins 6 (-) and 7 (+) and its output on pin 1. Then note that comparator 3 is the same on the other side of the IC, except for the polarity of the pins. Once you become familiar with the symmetry of the pin-out, you'll find working with the device quick and easy!

For simplicity, we are going to describe the logic probe in two parts, and we'll start with level detection first.

Beginning with the comparator inputs, there are two voltage dividers at work. The first uses  $R1 = 18k$ , and  $R2 = 10k$ , to set the logic probe voltage when not connected, to  $V_{cc} \times (10k / (10k + 18k))$  volts. When the rail voltage is 5V, the probe will be  $\sim 1.78V$ , or between 0.8V and 2.0V, so neither LED should be lit. The probe voltage is connected to the comparator inputs on pins 5 and 6, via two 100k resistors,  $R3$  and  $R4$ . You'll note that another 100k,  $R14$ , takes the probe voltage to pin 10 for the pulse circuit. We'll explain that section later.

When the rail voltage is 3.3V, the probe will be  $\sim 1.2V$ , so as before neither LED should be lit, and 3v3 TTL can be tested without issue.

For a CMOS circuit, two resistors of the same value should be used for  $R1$  and  $R2$ , but the values used for TTL will also work on CMOS, and no changes are necessary.

The second voltage divider chain using  $R3$ ,  $R4$  and  $R5$ , set the two reference values, 0.8V for "0" level TTL on comparator pin 4, and 2V for "1" level TTL on comparator pin 7. The string is designed for 5V TTL but works on 3v3 TTL with a little error in the absolute threshold values. For standard 5V TTL,  $R5 = 18k$ ,  $R6 = 8k2$  and  $R7 = 4k7$  respectively giving reference values at pin 4 of 775mV, and 2.04V on pin 7.

The switch allows the user to swap between two references: standard TTL in the forward position, and a second option in the back position. Assuming CMOS is the second option, the resistors should be  $R20=R6=R21 = 8k2$ . If you want a more exact reference for working on 3v3 TTL,  $R6$  remains as 8k2, as it is common to both switch positions and both options of CMOS and 3v3 TTL. Use a 10K for  $R20$ , and 5k6 for  $R21$ , only if you intend the second switch position to be used for 3v3 TTL.

## CONSTANT CURRENT LED DRIVE

The LEDs on the outputs of the comparators are on pin 1 ("1") and pin 2 ("0"). To keep the brightness of the LEDs about the same from 3V to 15V, a constant current source has been built using  $D1$ ,  $D2$ ,  $Q1$ ,  $R10$  and  $R11$ .  $R10$  limits the current to 20mA, but the supply is shared between LED 1 and LED2 as they do not come on together.

## REVERSE SUPPLY VOLTAGE PROTECTION

In the dreaded situation where a technically-minded person connects the red wire to ground and the black wire to 5V (as happens from time to time),  $R22$  and  $D3$  limit the reverse voltage >>

» across the LM339 to -0.6V, but R22 will start burning out and letting the smoke out; so consider it a sacrificial fused resistor!

## THE PULSE CIRCUIT

The pulse detector has a basic function in what it can do, as we wanted to keep the logic probe simple. In reality, it did start to collect more parts than originally intended. The basic circuit configuration is a monostable multi-vibrator (a name that takes up more space than the actual circuit!). Put simply, a brief trigger at the input, causes the output to turn on for a timed period.

We begin at the probe, where we are more interested in the change in voltage than the actual voltage. Therefore R14, another 100k is connected to pin 10 via C2, a 1 nanoFarad capacitor. The capacitor will only pass a current when the voltage is changing.

R12, 1M0 and R13, 100k set up a reference voltage on pin 10 of about 450mV. Comparator pin 11, due to the voltage divider using R8, 1M0, and R9, 68k, has a set value of about 290mV, for reasons we'll get to later in the loop!

The output of comparator 3 remains off in normal conditions. When the pulse of current presents at pin 10, it becomes temporarily more negative than pin 11 and it's output, pin 13 turns on which discharges C1. This turns comparator 4 off, which lifts the voltage on R9, so pin 11 is again higher than pin 10, turning comparator 3 off.

For comparator 4, R16, 220k and R17, 100k set pin 9 to about 1.6V, with some feedback from R18, 10M pulling pin 9 a little lower in normal times, but a little higher when the LED is on. This is positive feedback and serves as a Schmidt trigger, to add hysteresis to the switch.

Pin 8 of comparator 4 has the RC timing circuit using R15, 1M0, and C1, 1uF. The timing constant of this pair is 1 second, for 63% of the supply voltage. However, pin 8 is compared to the voltage on pin 9, ~1.6V, so switches in about one-third of a second. A longer pulse would result if R16 were made 100k, for example.

So what happens to comparator 4, is comparator 3 grounds pin 8, turning the output transistor off.

Transistor Q2 is turned on by bias resistor R23, which has been reduced to 330Ω as Q2 was not turning completely off. It sounds wrong but comparator 4 output wasn't pulling the base of Q2 low enough.

The orange LED, LED3, has a simple ballast resistor, R19, 1k0, although it might have been powered by the constant current circuit, sharing current with the other LEDs.

C1 charges with the current flowing in from R15, until the voltage across C1 reaches the value on pin 9, and as soon as it exceeds that

value, comparator 4 turns on, grounding the base of Q2. Everything is back to starting position except that C1 will continue to charge until it reaches rail voltage. The circuit is ready for another pulse.

## ASSEMBLY

While this object can be built from proto board or similar, it will quickly end up as a rat's nest, so we recommend using a PCB or kit from one of the supporting suppliers. The PCB is shaped and sized so it will be a natural size to hold for testing a circuit, and the probe tip and LEDs are all at one end, while the power leads and switch are at the other end. So doing it this way means not only will you have somewhere to put the components, but you won't have to guess where the connections go!

## HOMEMADE PCB

The PCB was in fact designed as a single-sided board, and those keen enough can download the PCB pattern from the website. Just be sure to use the "single-sided" pattern, which has wider tracks and larger pads for easier hand-drilling. You will need only two links of wire on the top-side of the PCB.

For commercially available boards, double-sided PCBs are often the same price as single-sided boards, so the links are integrated into the PCB already. There's not a whole lot of spare space on the board, so it does make life a little easier.

## POWER

We did argue a little – but only between gentlemen – about options for the power supply. While a 9V battery would power it and be reasonably tidy, it also required voltage regulation and special consideration for CMOS above the supply voltage.

In the end any kind of battery was disqualified as unnecessary when the thing is used to test a powered circuit anyway. Using the supply from the "DUT" (device under test) is the norm for logic probes, as they don't require much current anyway.

Still there may be options. My own probe had the leads ripped off it once, so I used a speaker cable with a pair of IC clips. When everything was TTL in DIP ICs, I simply clipped onto pins 7 and 14, or whatever the supply pins for the ICs were. I still think that's the way for ICs with legs!



Those who work mainly on Arduino, Raspberry Pi and such, may prefer a pair of male pins or female sockets (PIN-header-style) to go straight onto the supply pins/sockets. Alternatively, you might like to use alligator clips, or even solder the wires onto the DUT power supply. Others may prefer having a USB plug and lead, and even use a USB plug pack. All these options can have the wires soldered directly into the PCB, or place a right-angle two-pin header into the power pads, and plug onto them with a two-way 0.1-inch socket. It all really comes down to what you intend to work on.

REF:	COMPONENTS:	JAYCAR
R1	1M8 Resistor	RR1654
R2	1M0 Resistor	RR0644
R3	100k Resistor	RR0620
R4	100k Resistor	RR0620
R5	18k Resistor	RR0602
R6	8k2 Resistor	RR0594
R7	4k7 Resistor	RR0588
R8	1M0 Resistor	RR0644
R9	68k Resistor	RR0616
R10	33R Resistor	RR0536
R11	1k0 Resistor	RR0572
R12	1M0 Resistor	RR0644
R13	100k Resistor	RR0620
R14	100k Resistor	RR0620
R15	1M0 Resistor	RR0644
R16	220k Resistor	RR0628
R17	100k Resistor	RR0620
R18	10M Resistor	RR0660
R19	1k0 Resistor	RR0572
R20	8k2 Resistor	RR0594
R21	8k2 Resistor	RR0594
R22	33R Resistor	RR0536
R23	330R Resistor	RR0560
C1	1µF Electrolytic 25V	RE6032
C2	1nF Capacitor MKT 100V	RM7010
D1	1N4148 Diode	ZR1100
D2	1N4148 Diode	ZR1100
D3	1N4004 Diode	ZR1004
LED1	Red LED 3mm	ZD0100
LED2	Green LED 3mm	ZD0120
LED3	Orange LED 3mm	ZD0119
Q1	BC557 Transistor PNP	ZT2164
Q2	BC547 Transistor PNP	ZT2152
IC1	LM339N Quad Comparator	ZL3339
S1	DPDT Switch	SS0823

REF:	OTHER HARDWARE:
PROBE	1-pin eg. Test Probe -or- Canvas Needle <b>Paperclip (trimmed)</b>
PWR	2-pin Pin Header, 2pin-RA, polarised, (optional)
PWR	2-pin Pin Header, 2pin socket header
PWR-clip	IC-Clip IC Pin Test Clip Red
PWR-clip	IC-Clip IC Pin Test Clip Black
PCB	DIY1709-1 Printed Circuit Board, DIY17091-1 <b>Jaycar PCB</b>
Dims	3.05" x 1.05" (88.9 x 26.7mm) (88.9 X 26.7MM)
Case	DIY1709-1-33D printed case, (see text)

*Note: Our part numbers may denote a pack of parts, such as resistors which are often sold in a pack. We have suggested probe-tip hardware and other methods. Kits sold for this project may contain other suitable hardware for this purpose, and may not precisely match this list.*

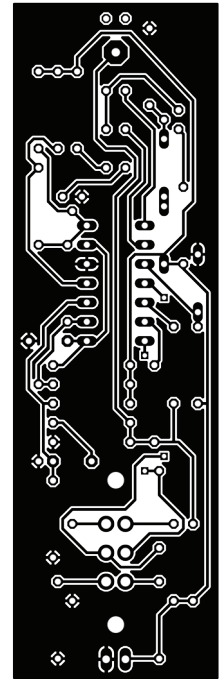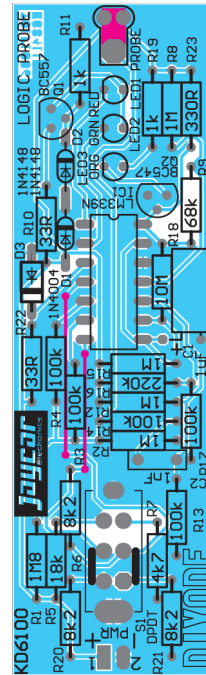You may choose to use a trimmed to size paperclip as probe tip.



#### GROUND LEAD

If you intend to use a dedicated power supply, which isn't connected to the DUT, the logic probe requires a ground lead that should be soldered in with the negative power wire, or onto the pad beneath the PCB. Using the DUT power supply avoids the requirement of a ground lead. This convenience is why we used DUT for power.

#### PROBE TIP

The kind of probe you use is dependent on your needs for the logic probe itself. You might want a good strong probe, or a tiny pin probe for getting into socket headers (for example). With this second user preference in mind, the PCB is made using a largish pad for a wire, with two smaller pads (not connected to ground) for a wire loop, to mechanically support the probe tip.

You may choose to use a trimmed to size paperclip as probe tip.

In the past, my TAFE students have used 1mm<sup>2</sup> (and bigger) electrician's copper wire, copper boat nails, darning needles, MIG welding wire, and many more clever solutions. One little known trick to make soft copper wire become hard, is to beat it with a hammer, rolling it as you go, so it remains basically round.

The hole in the end of the 3D printed case allows you to use a probe from an old multimeter lead, or a new one if you like. Sometimes it's handy to leave the probe connected to a wire, pin or circuit, so you can work hands-free. A short lead with an IC clip on one end and an alligator clip on the other can also be handy. Be inventive! >>

## » PCB ASSEMBLY

The usual rule for manual assembly is “hardware, passive, active”, meaning that you fit sockets, switches, and pins first. If you do use a two-pin header or whatever, or fit the power now, you can perform tests as you go, to make sure you have it all in the right places and soldered correctly.

So with the switch, probe and power soldered in, connect it up and check that you have 5V as expected, and where expected. It is a good practice to assemble in stages and test as you go, rather than loading up every component and soldering everything in one go.

### PASSIVE COMPONENTS

The resistors and capacitors come next, and a suggestion may be useful. If you think you might like to replace components at some stage, solder the component leads and cut them off close to the PCB. If you need to change one, it will be easier to get out.

The alternative, used in the industry and military, is to cut leads to about 1mm, bend them over, either flat against the PCB or at about 45 degrees, depending on just how harsh the mechanical forces on the PCB may be, and solder to cover the component pin as well as making the joint. This is a devil to remove without dedicated rework stations.

Make sure each joint is clean and shiny, and there are no “inclusions” (i.e., bits of nasty things unexpectedly stuck in the solder).

Out with the multimeter, and power up the circuit. There is a table provided with all the voltages to expect on the IC pads, for when the correct components are in the correct places, and are correctly soldered.

Compare your values to those in the table shown below.

CONDITION	NO IC	PROBE FLOATING	PROBE HI	PROBE LOW	PULSE LED OFF	PULSE LED ON
Pin 1	0.002	3.48	2	2.82	3.48	3.48
Pin 2	0	3.48	2.6	1.96	3.48	3.48
Pin 3	5.16	5.13				
Pin 4	0.795					
Pin 5	1.83	1.83	5.11	0.004	1.83	1.83
Pin 6	1.83	1.83	5.11	0.004	1.83	1.83
Pin 7	2.159					
Pin 8	4.7	1.586	1.586	1.575	1.586	0
Pin 9	1.84	1.61				
Pin 10	0.47	0.47	0.47	0.47	0.47	0.47
Pin 11	5.13	0.938	0.938	0.938	0.938	0.938
Pin 12	0	0				
Pin 13	4.7	1.587	1.586	1.586	1.586	0
Pin 14	5.16	0.651	0.29	0.29	0.29	0.29

## ACTIVE COMPONENTS

Active components are the most sensitive to heat and static electricity, so they should be left until last.

Place and solder the diodes and transistors, as well as the LEDs, but leave the IC until later. Be very careful with the active components – make sure you have the polarity correct. Check all the connections as above, and then check the voltages.

Use a small piece of wire to short the pads of pins 1, 2 and 14, to the ground, pin 12. Each of the LEDs should light: LED 1 and LED 2 when the short is in place, and LED 3 when it is not in place. This has also tested the constant current transistor Q1, and transistor Q2.



### LM339 PLACEMENT

The LM339 quad comparator IC is fairly robust, and the PCB has some basic protection against reverse voltage, but if you are unsure about your soldering, you might like to use a low profile IC socket. This way you can make sure your soldering is clean and tidy, no shorts, whiskers, or dry joints, and then fit the 14-pin IC. The dimple near pin 1 (i.e., the little curved bit taken out of one end), goes where the little bite is taken out of the overlay print. Don't laugh – even us old hands do it wrong sometimes!
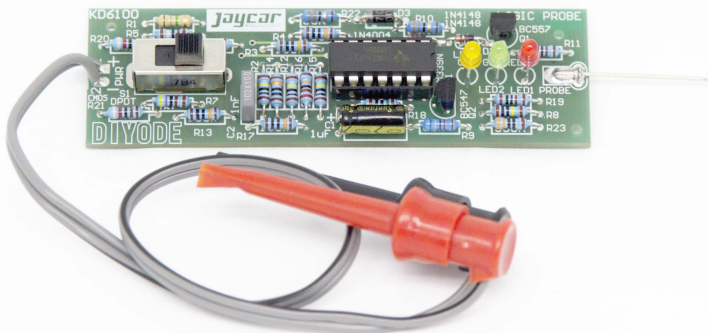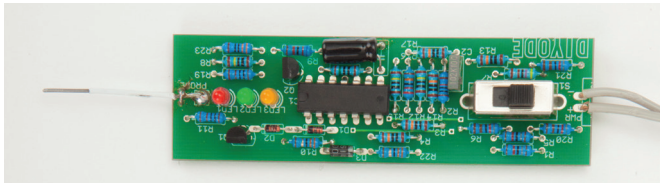
### FINALLY!

The big moment has arrived, and if you have passed all the tests so far, you should be looking at success. Power up, and nothing should happen – especially, no smoke. With a piece of jumper wire attached to the probe tip, touch pin 3 and the red LED should light. The orange LED should also come on briefly, about one-third of a second. Touch the ground, pin 12, and the green LED should come on. Note: I could have told you to put the switch in the forward position, but it doesn't really matter if we're looking for a good ground or positive rail.





## LEVEL TESTING FIELD

If you really want to, you can check your actual levels by putting a potentiometer between ground and 5V, and the probe on the wiper pin, and adjust until the green “0” LED just goes out. Read, and record the voltage, and then adjust until it just turns on; then read and record again, and see how much hysteresis there is. Note that no hysteresis is actually designed into the circuit, on the levels at least.

Likewise, adjust until the red “1” LED just comes on, read the voltage and record, and then adjust it until it just goes off; then read and record again. The values should not be very different, and should be less than 0.8V for a logic “0”, and more than 2V for a logic “1”; this is with the switch in the TTL position.

You can try it also in the CMOS position, and for different voltage supplies up to 15V. Low should be about one-third supply voltage, and high should be about two-thirds supply voltage.

## 3D PRINTED CASE

We have designed a handy case for mounting the probe, so it can easily become part of your toolkit.

The case has two snap-ins to hold the PCB in place, while the case halves snap together for a neat fit. The case may want to stay that way, so make sure you’re ready to leave it together, or perhaps sand the snap-ins so it goes together easily, and therefore comes apart easily. If the PCB is tight, it forces the sides of the case out, so make sure the PCB fits well before tackling the lid. Checking you have no protrusions from your PCB will help ensure a neat fit too.

It could be perpetually fine tuned, but PCB manufacturers will vary, and some of the “fit” depends on the 3D printer and how it is set up. The original case was designed in OpenSCAD, and we’ve provided the SCAD file to make any changes relatively easily too. For those of you using Tinkercad or similar software, you can easily import the STL file and add/remove shapes from the core design too, though some modifications are much easier to make in OpenSCAD as it can re-render the shapes from scratch.

## USING YOUR NEW PROBE

Obviously one caveat we must make is to never use this logic probe on voltages above 15V, or any device that runs on live ac current. IT IS NOT CatIII-rated, and isn’t meant to be. It’s meant for TTL / logic levels only.

Now that we’ve clarified that point, take a probe around a running Arduino or such. Using the DUT’s power supply avoids requiring a ground wire, and the probe has enough input resistance to be kind to your circuits.

If you strike a test point that doesn’t light, or lights intermittently either high or low, but doesn’t hold at least one LED on, then it is probably spending a lot of time in between a logic high and a logic low, or has a high impedance. Either way, you may have found your fault!

Logic probes take a little learning before you really know how to use one well, but once you get your proficiency badge, you’ll always have that skill in your kit. >>

## » ADVANCED TESTING - ARDUINO

If this is the first time you've used a logic probe, some advanced testing might be worthwhile to fully appreciate the relationship between the logic levels in your code (or created by an integrated circuit), and the actual levels and voltages presented in a circuit.

For this reason, we have created a basic Arduino Sketch, which you can use as a powerful test tool. It will also put your probe through its paces in an Arduino specific environment.

The sketch is quite simple, and you can elaborate on it further to test all pins. This is also a valuable education exercise.

```
int lowPin = 5;
int highPin = 6;
int pwmPin = 9;
void setup() {
  // set these pins as outputs
  pinMode(highPin, OUTPUT);
  pinMode(lowPin, OUTPUT);
}
void loop() {
  digitalWrite(highPin, HIGH);
  digitalWrite(lowPin, LOW);
  analogWrite(pwmPin, 10);
}
```


What we have effectively done here is quite simply, set pin 5 to LOW, pin 6 to HIGH, and pin 9 (which is a PWM-enabled hardware pin) to a low value.

You may notice that in the setup function, we have specified our high and low logic pins as OUTPUT, but not our PWM pin. This is because the analogWrite function does this automatically.

It's important to remember to use the pinMode function in setup for any standard digital outputs.

We have also included this sketch as probe\_test.ino in the digital resources too. Load the sketch onto your Arduino.

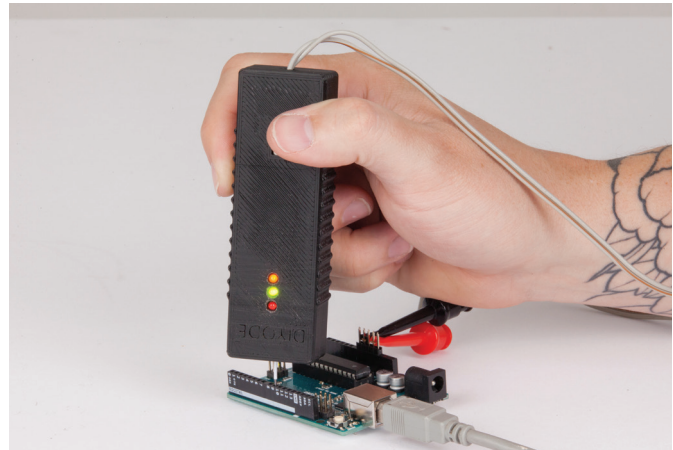Connect power for your probe to the 5V and GND pins on your Arduino. While you should have performed basic tests on your probe already, if you want to be sure your probe is working, you can touch the probe tip onto the 5V or GND. You should see the red or green LEDs illuminate respectively. As long as this occurs, move on to the pins we have specified in the sketch.



**LOW:** Touch the probe tip to pin 5, which we have set with a LOW output. You should see the green LED illuminate.

**HIGH:** Touch the probe tip to pin 6, which we have set with a HIGH output. You should see the red LED illuminate.

**PULSE:** Touch the probe tip to pin 9, which we have set with a PWM output.

You may also notice that the green LED is illuminated. This is because we have set it to around 4% duty-cycle (more accurately, 10/255, or 0.3921... but who's counting). This is because the probe features some great functionality. When a pulse width output is detected, the red and green LEDs act as a duty-cycle reference. When the duty cycle is low (that is, off more often than on), the green LED will illuminate alongside the yellow pulse indicator.

```
int ledPin = 9;
void setup() {
  // nothing happens in setup
}
void loop() {
  // fade in from min to max in increments of 5
  for (int fade = 0 ; fade <= 255; fade += 5) {
    // sets the value (range from 0 to 255):
    analogWrite(ledPin, fade);
    // wait 300ms to see the dimming effect
    delay(300);
  }
  // fade out from max to min in increments of 5
  for (int fade = 255 ; fade >= 0; fade -= 5) {
    // sets the value (range from 0 to 255):
    analogWrite(ledPin, fade);
    // wait 300ms to see the dimming effect
    delay(300);
  }
}
```

Likewise when the duty cycle is high (that is, on more often than off), the red LED will illuminate alongside the yellow pulse indicator. Of course, when the pulse width is somewhere in between, you will see all three LEDs illuminated.

Component tolerances will affect the precise points where the high and low LEDs switch on and off when the probe is in pulse mode. However, to demonstrate this, we can utilise a modified version of the FADING example sketch included with the Arduino IDE. Ours is not too different from the example provided with the software, however we have slowed the cycle down considerably so it's more visible and you can watch it go through the full cycle from 0% to 100% duty cycle, and back again. This sketch is provided in the resources as `probe_pwm_cycle.ino`. Load it onto your UNO and touch the probe to pin 9, watching what happens!

## WHAT ABOUT A RASPBERRY PI?

The beauty of logic is that it's, well - logical. The process for coding a similar test on Raspberry Pi is fairly similar. But we've done it for you, providing the sample Python scripts in the resources.

Of course, you still need to tell the Raspberry Pi what you're doing, and set the various pins to have their respective outputs.


Here is a basic Python code to achieve something fairly similar to `probe_test.ino`, but it's Python so we'll call it `probe_test.py` (i know, we're very creative).

Load `probe_test.py` in IDLE and run. Since Raspberry Pi pins are unlabelled, it's easiest to use a GPIO breakout adaptor which provides full labels on each of the pins.

Again, you can verify your probe is powered and working properly by touching the tip to any of the GND or 5V pins on the Pi, and looking for the green or red lights respectively.

```
import RPi.GPIO as GPIO
GPIO.setmode(GPIO.BCM)
lowPin = 5
highPin = 6
pwmPin = 13
GPIO.setup(lowPin, GPIO.OUT) # set up pin 17
GPIO.setup(highPin, GPIO.OUT) # set up pin 18
PWM1 = GPIO.PWM(13, 100) # enable software PWM
GPIO.output(lowPin, 0) # send pin 5 low
GPIO.output(highPin, 1) # send pin 6 high
PWM1.start(10) # start PWM at 10%
```

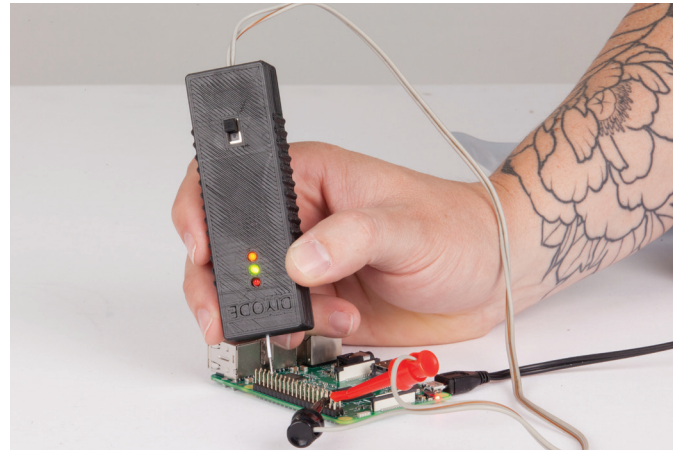As in the Arduino examples, we'll also provide an example for a cycling PWM output so you can see the effect it has on the probe. Load and run `probe_pwm_cycle.py`. Pin 13 should start looping



through the cycle taking it from 0% duty cycle to 100% duty cycle, and continue on forever (well, until you forcibly quit the programme).

The interesting thing about Raspberry Pi PWM is that there's only two hardware PWM channels. Most PWM functionality is derived from software PWM via the GPIO library. For most purposes, it's perfectly adequate and opens up far more functionality than would otherwise be provided for this purpose.

```
import RPi.GPIO as GPIO
GPIO.setmode(GPIO.BCM)
PWM1 = GPIO.PWM(13, 100) # enable PWM at 100Hz
PWM1.start(0) # start PWM at 0%
while 1:
    for level in range(0, 101, 5):
        p.ChangeDutyCycle(level)
        time.sleep(0.5)
    for level in range(100, -1, -5):
        p.ChangeDutyCycle(level)
        time.sleep(0.5)
```

So there you have it! Go forth and conquer logic with your new logic probe, and newfound understanding of how it works! ■

## WANT MORE?

For additional code, or to discuss this project, visit:  
<https://diyode.io/004tdqg>

## Buy The Logic Probe Kit:

► JAYCAR  
KD6100

[www.jaycar.com.au](http://www.jaycar.com.au)

## COMPONENT IDENTIFICATION

This section will help you to match some of the symbols used in schematics (electronic circuit diagrams) to the physical component used in the actual product. You will see the symbol on the left and the component on the right.

### RESISTORS

Symbol	Component
	4 or 5 Band ¼ or ½ Watt
	1 Watt
	5W or 10W Ceramic

### VARIABLE RESISTORS

Symbol	Component	Symbol	Component
	Trimpot		Potentiometer

### CAPACITORS

Symbol	Component
	Non-Polarised
	Ceramic
	MKT
	Greencap
	Non-Polarised Electrolytic
	Polarised
	Electrolytic
	Tantalum

### DIODE / ZENER DIODE

Symbol	Component
	Diode
	Zener Diode

### BRIDGE RECTIFIER

Symbol	Component
	Bridge Rectifier

## COMPONENT IDENTIFICATION

### LED's

Symbol	Component
	LED

### INTEGRATED CIRCUIT (IC)

Symbol (example)	Component
	IC Component

Pin 1 (to the left of cutout or mark on IC)

### TRANSISTORS

Symbol	Component
	(FET) TO-3
	TO-92 Body has pin assignments depending on the sub type indicated in brackets.
	TO-92 (72)
	TO-18
	TO-220
	TO-220(A)

## COMPONENT IDENTIFICATION

	LAMP		FUSES
	MICROPHONE		CRYSTAL
	BATTERY		

## COMPONENT IDENTIFICATION

### VOLTAGE REGULATORS

#### VOLTAGE REGULATORS

Component	Symbol
	POSITIVE REGULATOR TO-220 PACKAGE 78XX, LM340, LM2940
	NEGATIVE REGULATOR TO-220 PACKAGE 79XX, LM320
	POSITIVE ADJUSTABLE REGULATOR TO-220 PACKAGE LM317, LM350
	NEGATIVE ADJUSTABLE REGULATOR TO-220 PACKAGE LM337
	POSITIVE REGULATOR TO-3 PACKAGE 78XX, LM340
	NEGATIVE REGULATOR TO-3 PACKAGE 79XX, LM320
	ADJUSTABLE REGULATOR TO-3 PACKAGE LM317, LM350
	POSITIVE REGULATOR TO-92 PACKAGE 78LXX

### OHM'S LAW

The most basic law in electronics. The relationship between resistance, voltage and current is determined by Ohm's Law (\*). If you know two out of the three values you can work out the third.

$$V = I \times R$$

$$I = V / R$$

$$R = V / I$$



The formulas are:

V is Voltage  
I is Current in Amps and  
R is resistance in Ohms

**Jaycar**  
Electronics


No 1 for Kits

kits@jaycar.com.au

COMPONENT REFERENCE CHART

Ver 1.2 - 24.03.2010

## RESISTOR COLOUR CODES

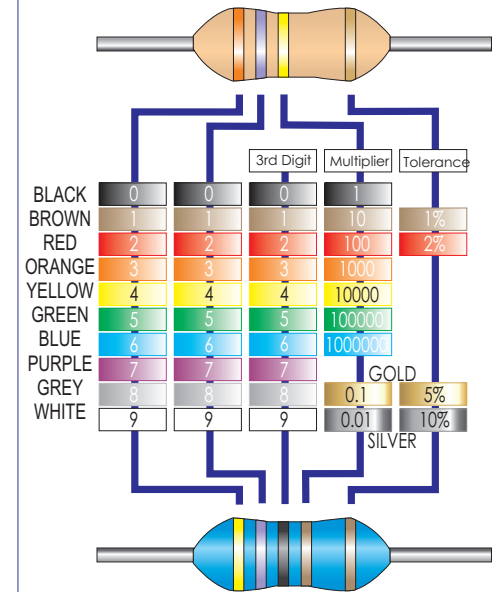

Examples:

(5 BAND)  
yellow-purple-black-brown-brown  
= 4 - 7 - 0 - 1 - 1% = 4K7 1%

(4 BAND)  
orange-purple-yellow-gold  
= 3 - 7 - 4 - 10% = 370K 10%

## CAPACITOR CODES

Microfarads (u)	Nanofarads (n)	Picofarads (p)	EIA code
-	-	100pF	101
-	0.22nF	220pF	221
0.001uF	1nF	1000pF	102
0.0047uF	4.7nF	4700pF	472
0.01uF	10nF	-	103
0.047uF	47nF	-	473
0.1uF	100nF	-	104
0.47uF	470nF	-	474
1uF	1000nF	-	105

## ZENER DIODES (1 WATT UNLESS SPECIFIED)

Part no.	Voltage	Part no.	Voltage
1N4728	3V3	1N4744	15V
1N4729	3V6	1N4745	16V
1N4730	3V9	1N4746	18V
1N4731	4V3	1N4747	20V
1N4732	4V7	1N4748	22V
1N4733	5V1	1N4749	24V
1N4734	5V6	1N4750	27V
1N4735	6V2	1N4751	30V
1N4736	6V8	1N4752	33V
1N4737	7V5	1N4753	36V
1N4738	8V2	1N4754	39V
1N4739	9V1	1N4761	75V
1N4740	10V	1N5349B	12V 5W
1N4741	11V	1N5352N	15V 5W
1N4742	12V	1N5374	75V 5W
1N4743	13V		